

Sign in - Google Accounts   Circuit design Terrific Jarv-Juttuli   WhatsApp   Ask Gemini

tinkercad.com/things/99PER6kZLxm/editel?returnTo=%2Fdashboard

Ask Google   Verify it's you

Terrific Jarv-Juttuli   Circuits   Schematic   Components

Simulator time: 00:00:02

Code   Stop Simulation   Send To

Components Basic

led

LED   LED RGB

Other Components

NeoPixel   NeoPixel Ring 12   NeoPixel Ring 16

NeoPixel Ring 24   NeoPixel Strip 4   NeoPixel Strip 6

NeoPixel Strip 8   NeoPixel Strip 10   NeoPixel Strip 12

The image shows a Tinkercad circuit simulation. An Arduino Uno is connected to a breadboard. On the breadboard, there is a light sensor module (likely a photoresistor) and an LED. Wires connect the sensor to the Arduino's analog input pins and the LED to the digital output pins. A 16x2 LCD display is also connected, showing the ADC value and the status. The right sidebar displays the 'Components' panel with a search for 'led' and various LED options like NeoPixel and NeoPixel Ring. The bottom status bar shows the system temperature as 33°C and the time as 12:37 on 02-10-2026.

Sign in - Google Accounts   Circuit design Terrific Jarv-Juttuli   WhatsApp   Ask Gemini

tinkercad.com/things/99PER6kZLxm/editel?returnTo=%2Fdashboard

Ask Google   Verify it's you

Terrific Jarv-Juttuli

Circuits   Schematic   Components

Simulator time: 00:00:10

Code   Stop Simulation   Send To

Components Basic

led

LED   LED RGB

Other Components

NeoPixel   NeoPixel Ring 12   NeoPixel Ring 16

NeoPixel Ring 24   NeoPixel Strip 4   NeoPixel Strip 6

NeoPixel Strip 8   NeoPixel Strip 10   NeoPixel Strip 12

The image shows a Tinkercad circuit simulation. An Arduino Uno is connected to a breadboard. On the breadboard, there is a photoresistor (labeled 'Photoresistor Name 1') and an LCD display. The LCD shows 'ADC: 425' and 'Status: NORMAL'. The photoresistor is connected to the breadboard and labeled 'Photoresistor Name 1'. The breadboard also contains a 10k resistor and a 100 ohm resistor. The Arduino is connected to the breadboard via its digital and power pins. The photoresistor is connected to the breadboard via its two pins. The LCD is connected to the breadboard via its four pins. The breadboard is connected to the Arduino via its power and ground pins. The photoresistor is connected to the breadboard via its two pins. The LCD is connected to the breadboard via its four pins. The breadboard is connected to the Arduino via its power and ground pins.

33°C Mostly sunny   Search   12:37 02-10-2026

Sign in - Google Accounts x Circuit design Terrific Jarv-Juttuli x WhatsApp x + Ask Gemini - x

tinkercad.com/things/99PER6kZLxm/editel?returnTo=%2Fdashboard

Ask Google Schematic Components Verify it's you

Terrific Jarv-Juttuli

Circuits Schematic Components

Simulator time: 00:00:17

Code Stop Simulation Send To

Components Basic

led

LED LED RGB

Other Components

NeoPixel NeoPixel Ring 12 NeoPixel Ring 16

NeoPixel Ring 24 NeoPixel Strip 4 NeoPixel Strip 6

NeoPixel Strip 8 NeoPixel Strip 10 NeoPixel Strip 12

33°C Mostly sunny 12:37 02-10-2026

The image shows a Tinkercad circuit simulation. An Arduino Uno is connected to a breadboard. On the breadboard, there is a photoresistor (labeled 'Name 1') and an LED. The LED is lit, indicating it is receiving power. The Arduino is connected to a breadboard with various components, including a photoresistor and an LED. The LED is lit, and the LCD display shows 'ADC: 663' and 'Status: BRIGHT'. The photoresistor is labeled 'Name 1'. The circuit is connected to a power source (5V and GND) on the Arduino. The breadboard also contains a 100 ohm resistor and a 10k ohm resistor. The photoresistor is connected to the 5V and GND pins of the Arduino. The LED is connected to the 5V and GND pins of the Arduino. The LCD display is connected to the Arduino via I2C. The status bar at the bottom shows a temperature of 33°C, mostly sunny weather, and the time 12:37 on 02-10-2026.